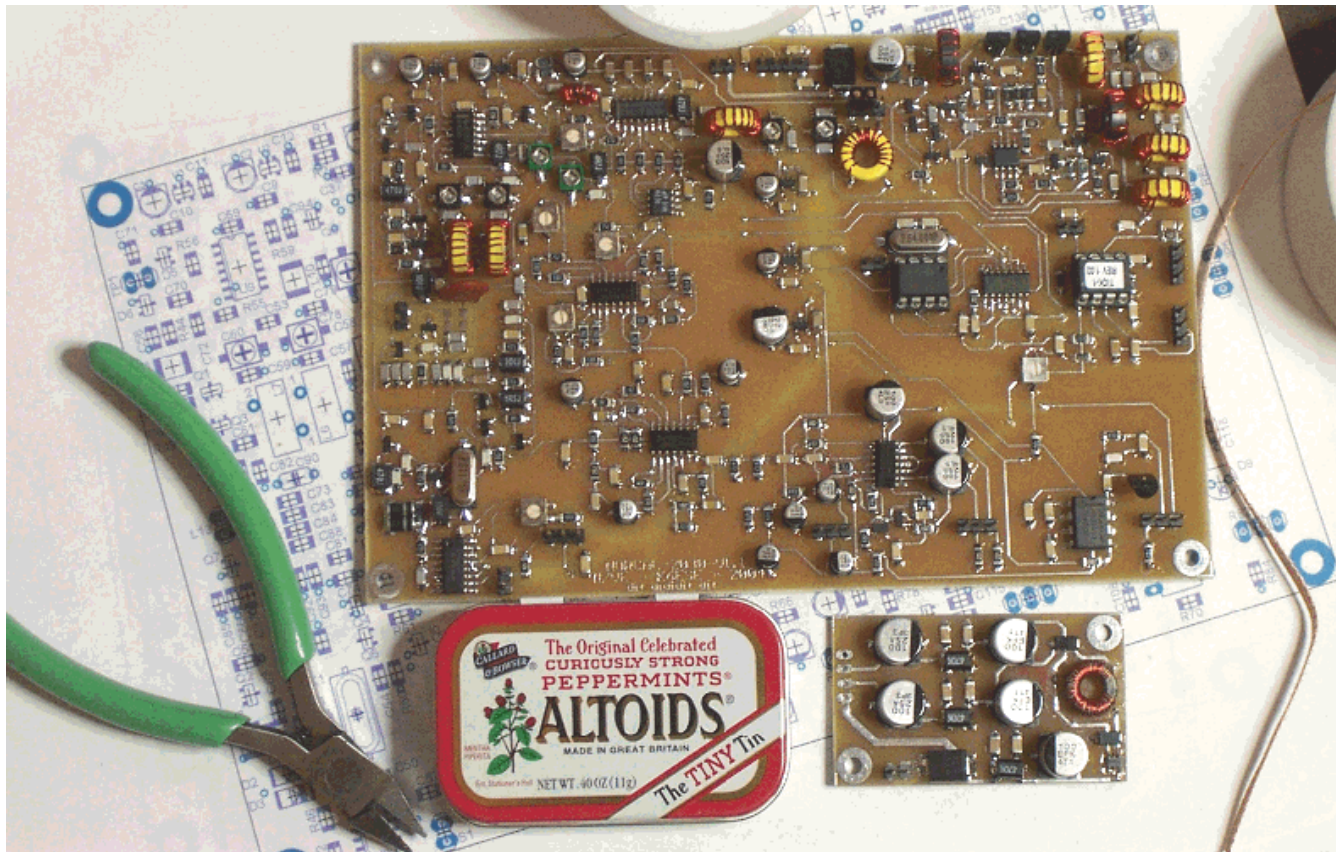



Very High Performance Image Rejecting Direct Conversion Receivers

*Or how can an 11 ma receiver out perform the world's best
ham transceivers?*



Dan Tayloe, N7VE

NC2030 20m Prototype

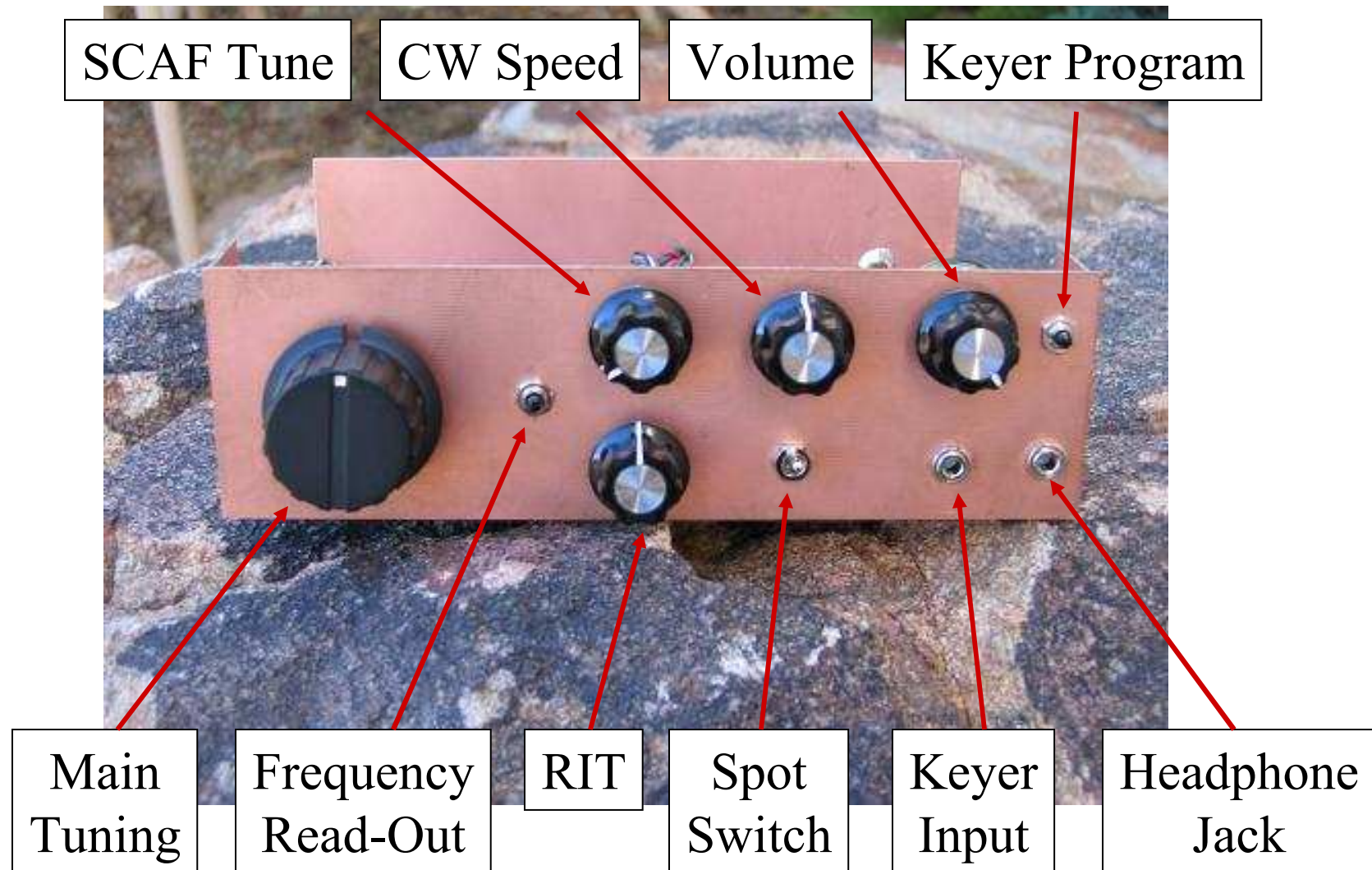


NC2030 Receiver Specs

- MDS (3db S+N/N): **-135 dbm** (0.1 uV)
- Receiver Bandwidth (-6db): **350-800 Hz**
- IP3 DR: **93db** (2KHz), **105 db** (5 KHz), **109 db** (10 KHz)
- BDR: **119db** (2 KHz), **128.5db** (5 KHz), **139db** (10 KHz), **142db** (20 KHz)
- Image rejection: ~ **>45 db over the band**
- Receiver current drain: ~ **11 ma at 12v**

BDR: A Comparison – 5 KHz

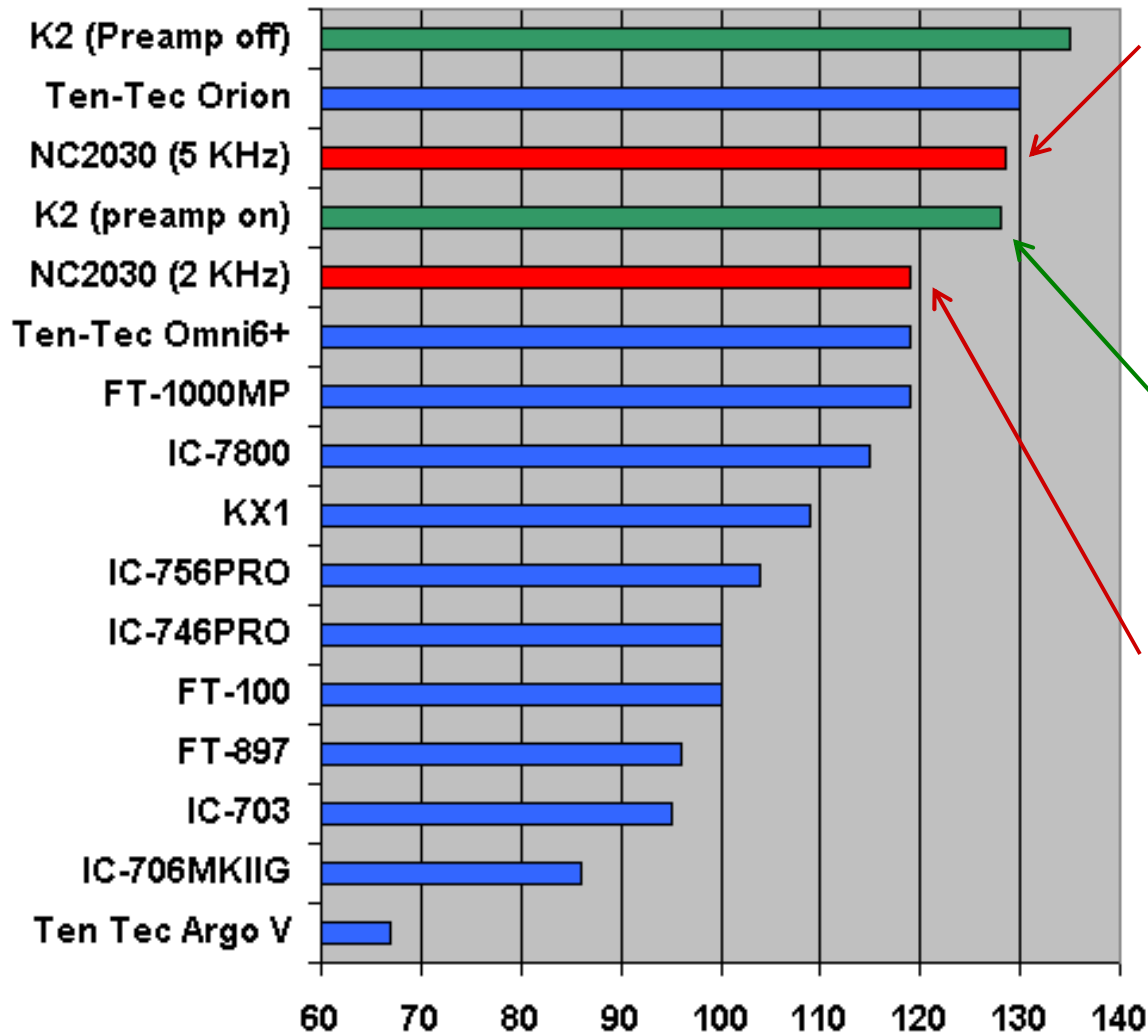Blocking Dynamic Range
(5 KHz spacing - Preamp Off)




NC2030 *at full sensitivity*, ranks among the best rigs which were measured with their RF pre-amps *off*.

Note: With the RF pre-amp on, the K2 suffers a 7 db degradation in blocking

Even at only *2 KHz*, the NC2030 performs at least as well as all but two rigs measured at *5 KHz*.

Blocking DR: A comparison (vs. K2)

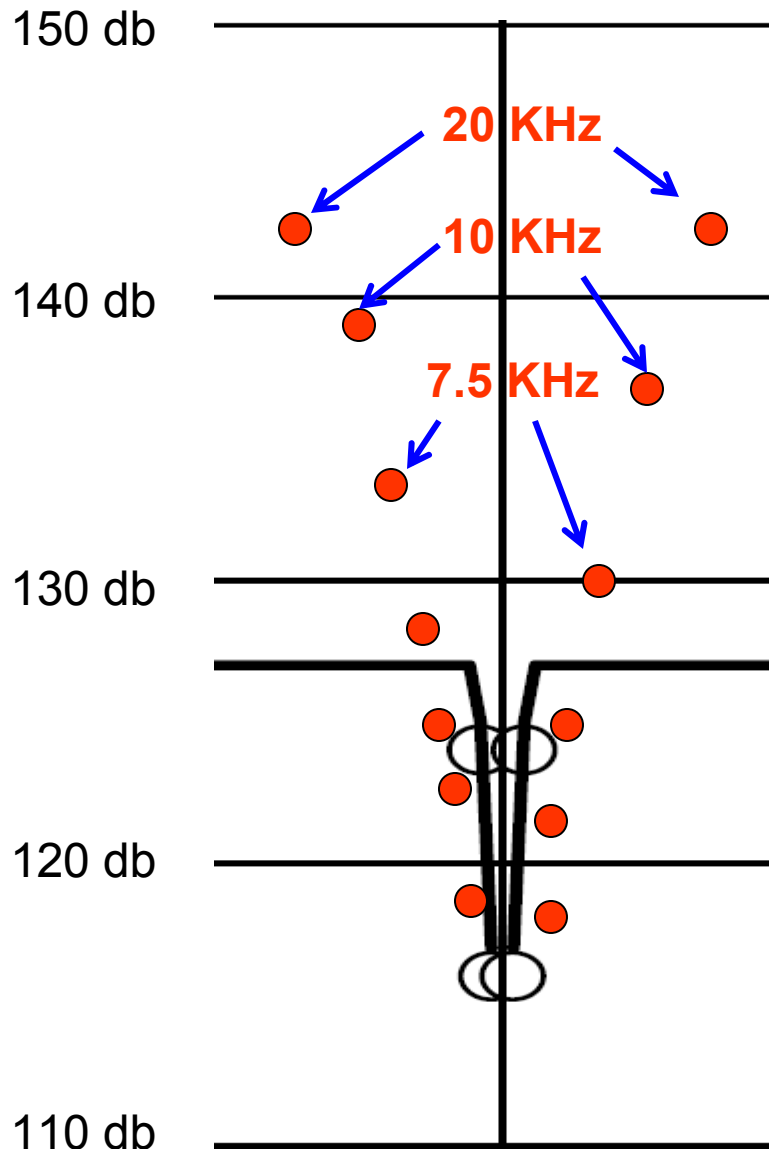

*Extracted from QST K2 expanded report

KHz	Low Side	High Side
2	119	
3	122	118
4	125.5	122
5	128.5	125
6	-	-
7	133	130
10	139	137
20	142	142


NC2030 Blocking DR does not plateau
- *Rejection keeps improving*

K2 plateau shows IF amp saturation
- *Signals on the other side of the band (300+ KHz away) can still cause blocking*

=> NC2030 blocking is a bit worse close in,
much better further out

IP3DR: A comparison – 5 KHz

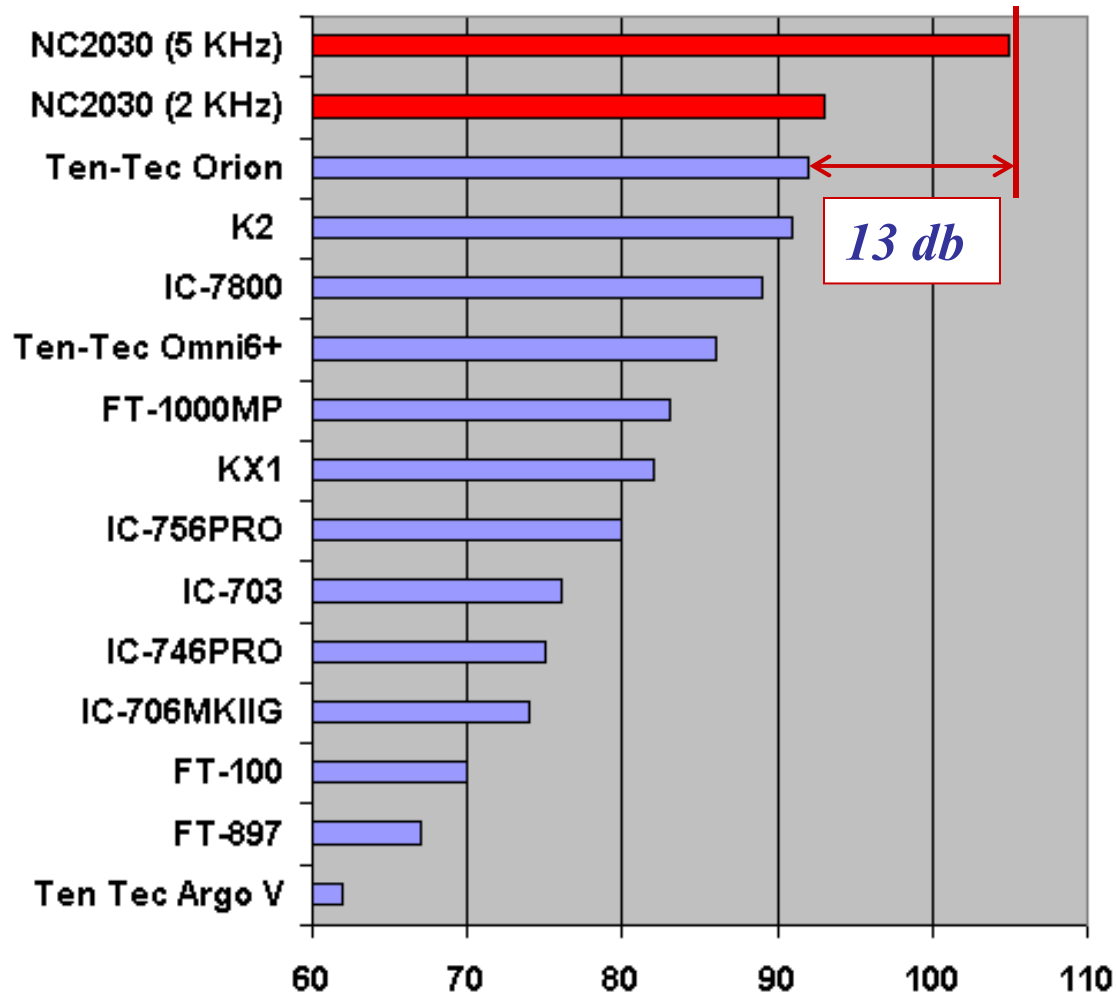Third order intercept Dynamic Range
(5 KHz spacing - Preamp Off)




NC2030 at **5 KHz** is **13 db** better than the best.

NC2030 at **2 KHz** is still better than all the rest at **5 KHz**.

Not a true apple-to-apples comparison since NC2030 is at **full sensitivity** while other rigs have **pre-amps off**

IP3 DR: A comparison (vs. K2)

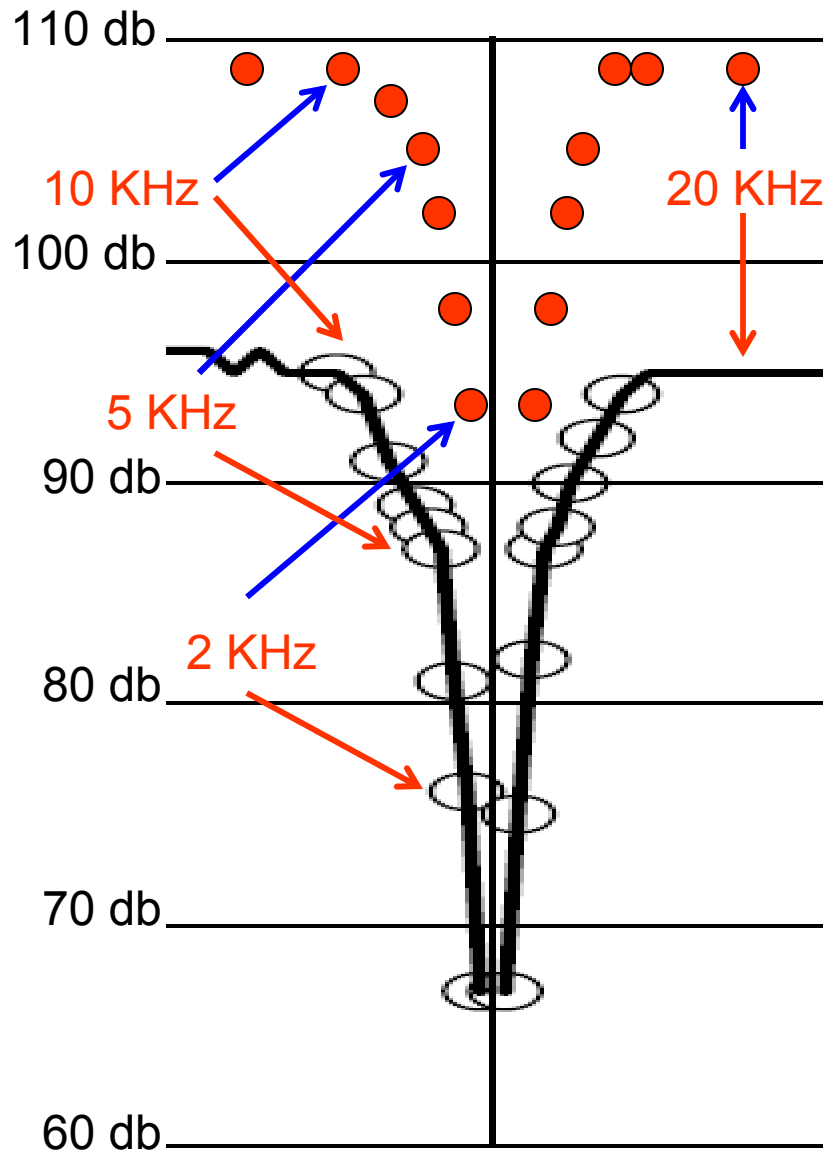

*Extracted from QST K2 expanded report


KHz	Low Side	High Side
2	93	-
3	98.5	93.5
4	102	98.5
5	105	102
6	-	106
7	107.5	109
10	109	109
20	109	109

IP3DR is *noticeably better* than the best radios available (K2/Orion)

NC2030 appears *17 db* better 2 KHz away (93 db vs. 76 db)


NC2030 appears *18 db* better 5 KHz away (105 db vs. 87 db)

Typical Superhet Front End

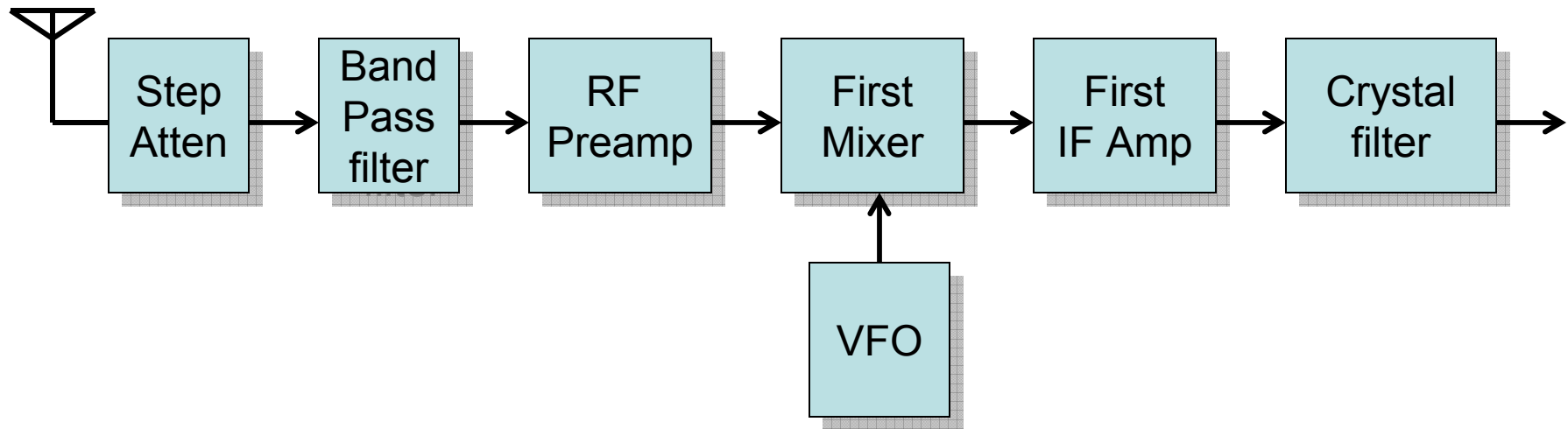


- This is a simplified view, but represents many superhet receiver front ends
- The **large signal performance** is set in the sections **before** the radio “brick wall” filtering (Xtal filter)

Superhet Front End Bandwidth

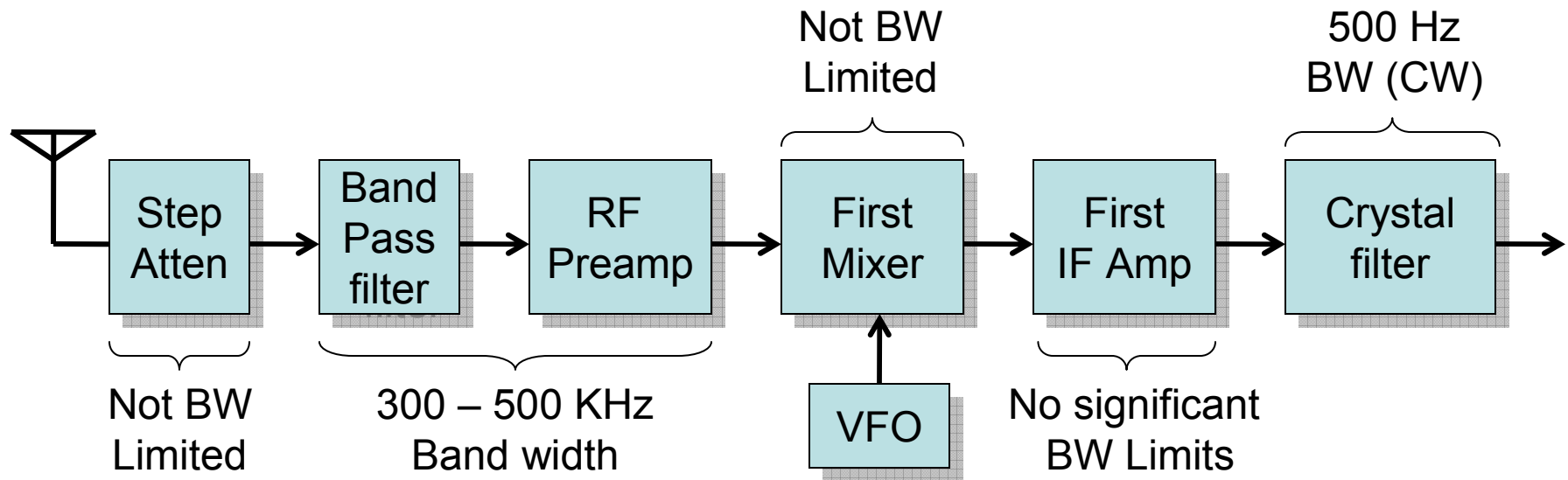


- RF preamp, first mixer, and first IF amp sees **all signals** in the **entire band** all at the same time.
- Wide front end bandwidth is the main reason **preamps are turned off** and **attenuators are kicked** in during a contest.

Phasing DC Front End

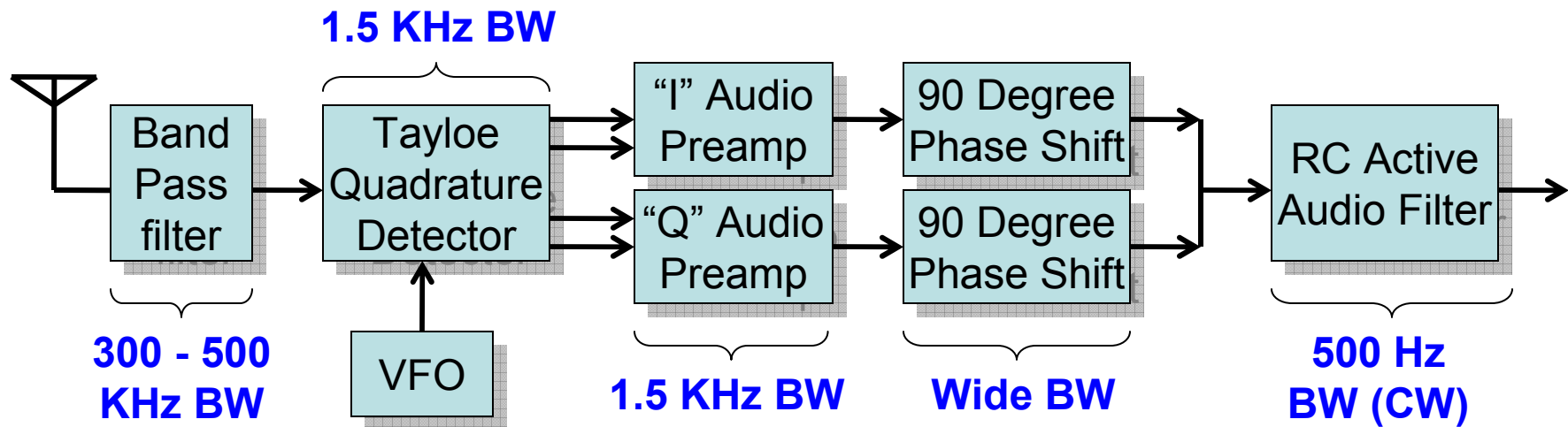


- The narrow bandwidth direct conversion detector allows ***few signals*** to get to the audio preamps.
- The audio preamps also has a narrow bandwidth, thus off frequency signals are ***attenuated even further*** prior to the receiver “brick wall” audio filter

Band View: Superhet Vs. DC RCVR

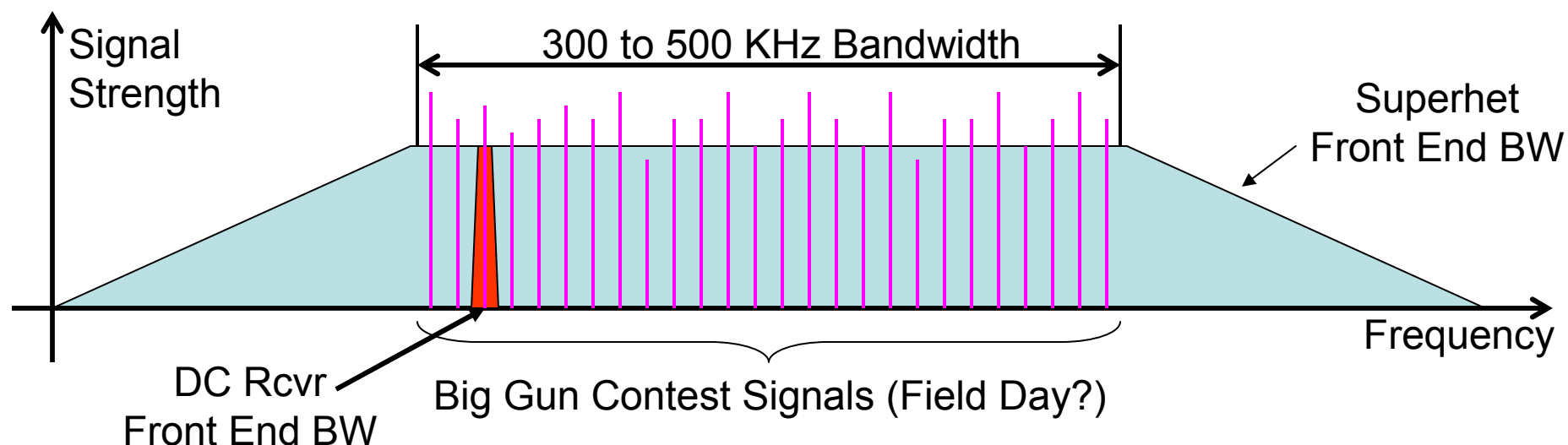


- Superhet RF preamp/Mixer/IF Amp **sees all signals at full strength**
 - Must remain linear with the **sum of all the signals on the band**
 - **This is hard!** RF pre-amp on/off, Attenuators, Variable IF amp gain
 - Requires a lot of power to stay linear; IF amp often uses **50 to 100 ma**
- DC receiver sees only a fraction of the band
 - Must remain linear over **just a few** of the many signals on the band
 - Only the close in signals are problems; **-16 db, 5 KHz** away, **-40 db** at **20 KHz**
 - **A much easier problem!**

Superhet RF/IF Preamps

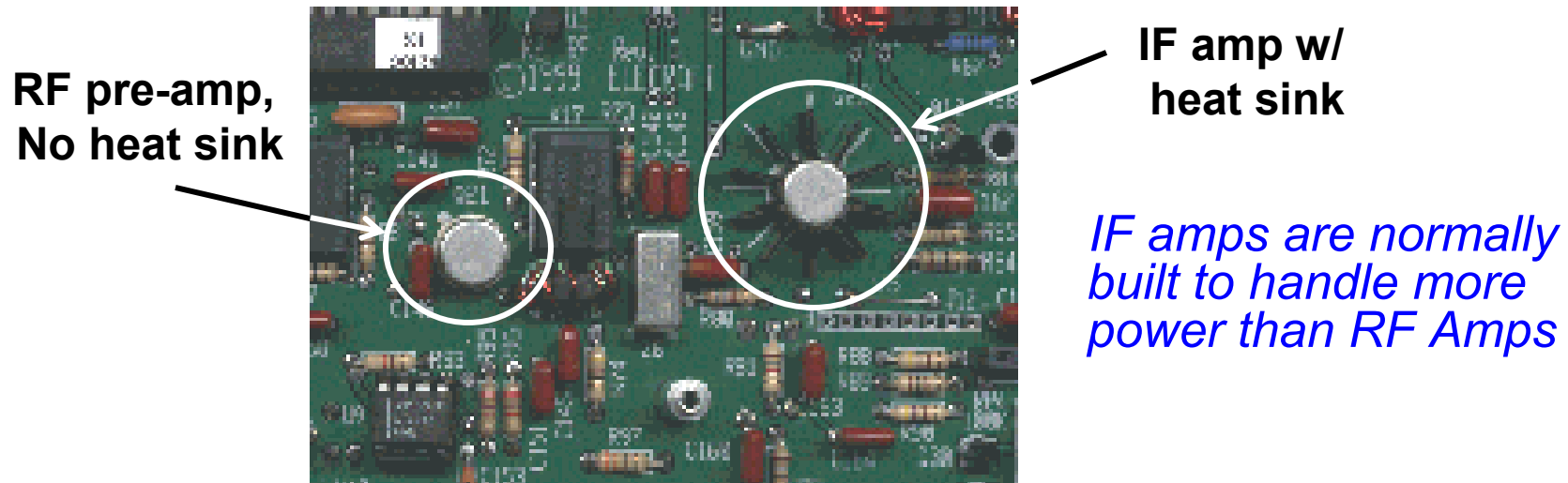


- RF and IF amps are typically 50 ohm in, and low Z out
 - These are both **power** amplifiers
- Wide band, high signal linearity amps require **lots of power**
- RF pre-amps are not normally designed to survive large in band signals
 - Which is why they are **useless** and **get turned off** in a contest
 - First mixer can only handle so much power out of RF preamp anyway
 - Superhet performance measured with **RF Preamp off** for a reason

DC Receiver Detector/AF Preamps

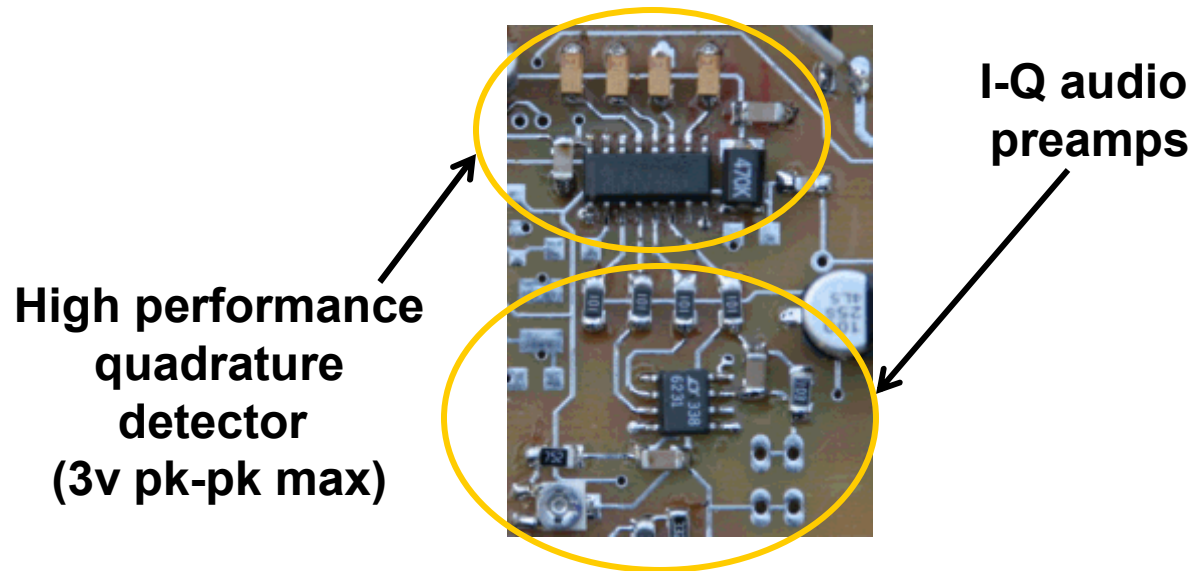

- Detector has ***~0.9 db*** of conversion loss rather than the typical high performance superhet ***6 to 8 db*** mixer loss
 - Thus, RF preamp ***not needed*** to overcome first mixer loss
 - Allows receiver to have both ***high sensitivity*** & ***large signal*** performance
- AF Pre-amp is low Z in, high Z out, ***voltage amplifier***
 - ***Voltage amplification*** takes less power than ***power amplification***
- Detector/AF preamp rolls off relatively quickly
 - ***16 db down at 5 KHz, 27 db at 10 KHz, 39 db at 20 KHz***


Superhet “Brick Wall” Filters

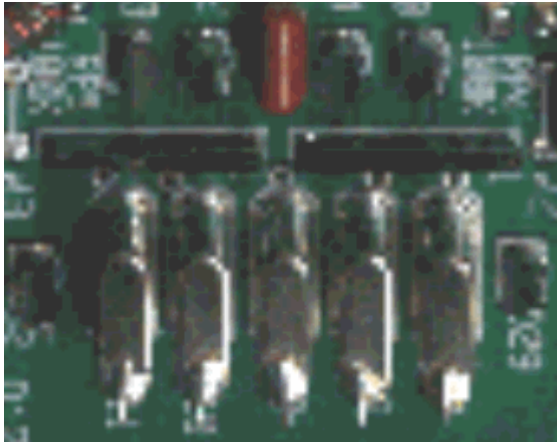

Typical crystal filter, 5 crystals

- RF preamps and IF amps must have power limits because of **crystal filter limitations**
- Crystals used in xtal filters typically **10 mW**
 - **~1.4v RF limit, blocking limit of ~140 db BDR**
- Crystal power limitations may contribute to **close in IP3 problems**
- **FT243 crystals might make superior filters**
 - **Old FT243 crystals handle much higher power levels**

DC Receiver “Brick Wall” Filters

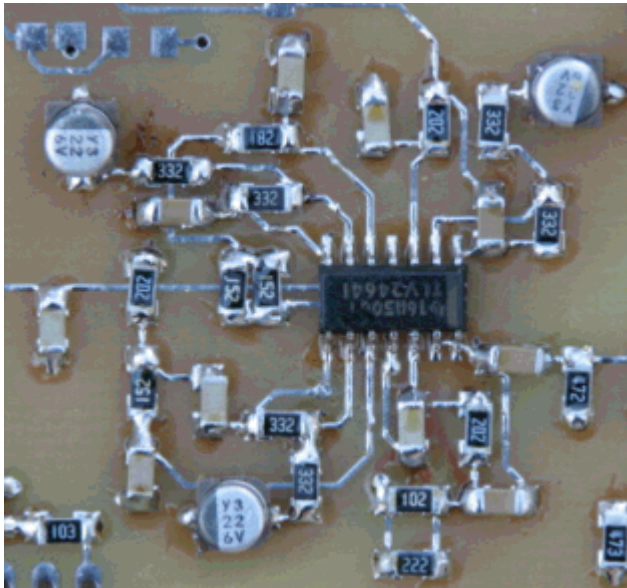


8 pole low pass filter

- NC2030 8 pole low pass filter
- High voltage, **very high dynamic range** “brick wall” RC filters are easily constructed

- Caps typically **50v**
- **1/2w** resistors common
- Op amps typically **+/- 18v (36v)**

- R/C filters: **Lots of Rs and Cs!**
- With a **3v** receiver chain, NC2030 has **~13 db better IP3DR** and **similar BDR** to the best available rigs
 - And this is at **full sensitivity**, not “RF Pre-amp off”!


Superhets can be simple

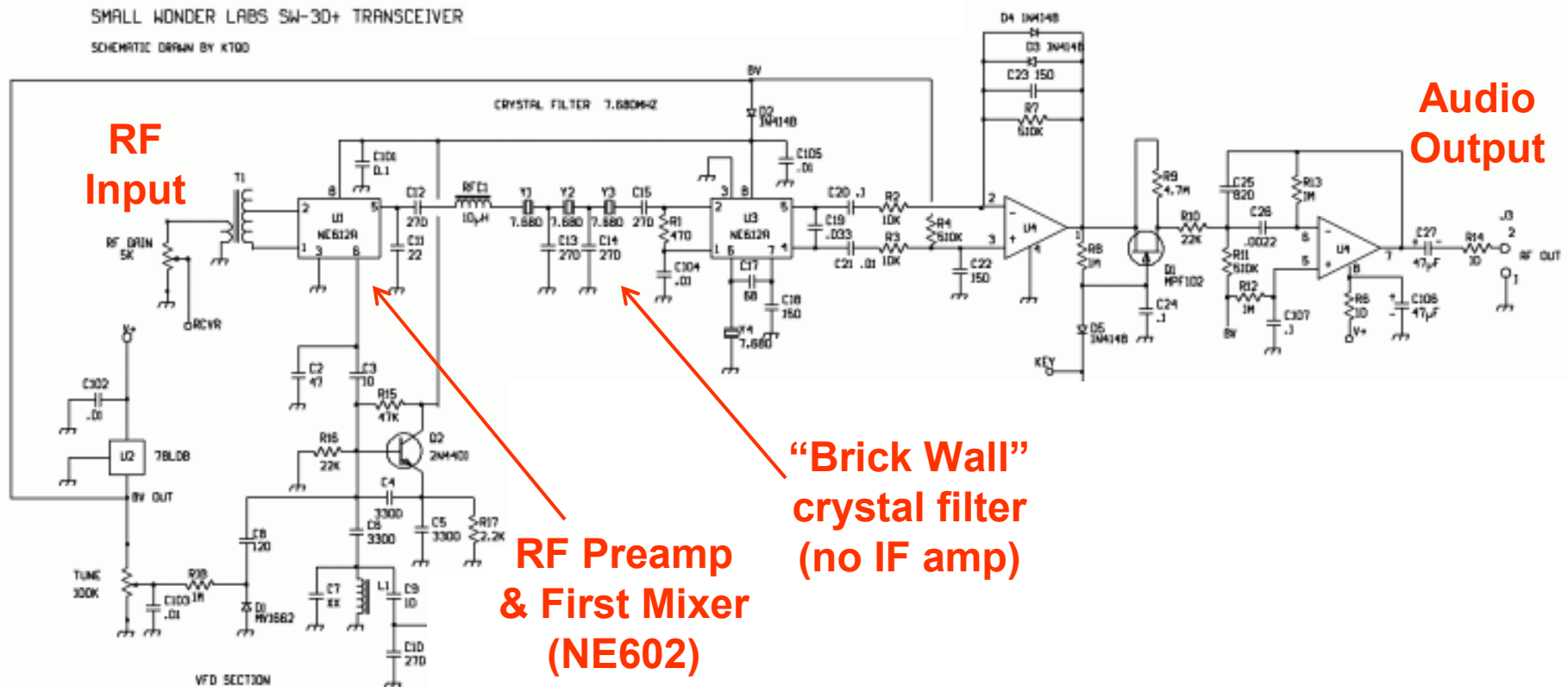

However, this is not a high performance superhet

DC Receivers can be simple also

“49er” Receiver Schematics

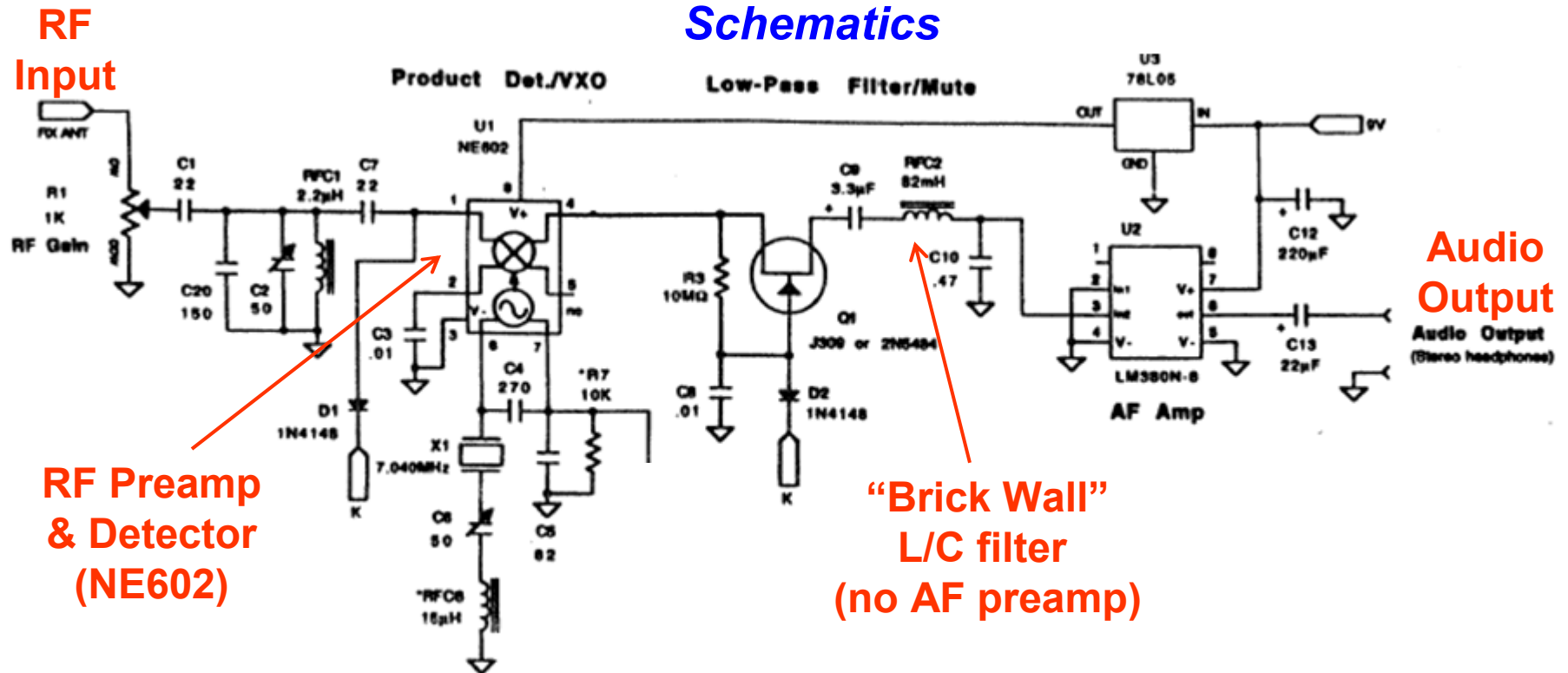

However, this is not a high performance DC Rcvr

A High Performance Phasing DC Receiver (NC2030) has a Price


Lots of parts, with many Rs and Cs!

- ~280 out of 360 total parts are Rs and Cs

- ***175 Capacitors***
- ***108 Resistors***
- 25 Inductors
- 19 ICs
 - 5 op amps, 5 LDO voltage regulators, 5 digital ICs, 2 uPs, 1 SCAF, and 1 switching regulator
- 17 Transistors
- 17 diodes
- 2 crystals


⇒ ***High performance DC Receiver (NC2030) is more complex than a typical superhet***

- ***But higher performance and less power!***

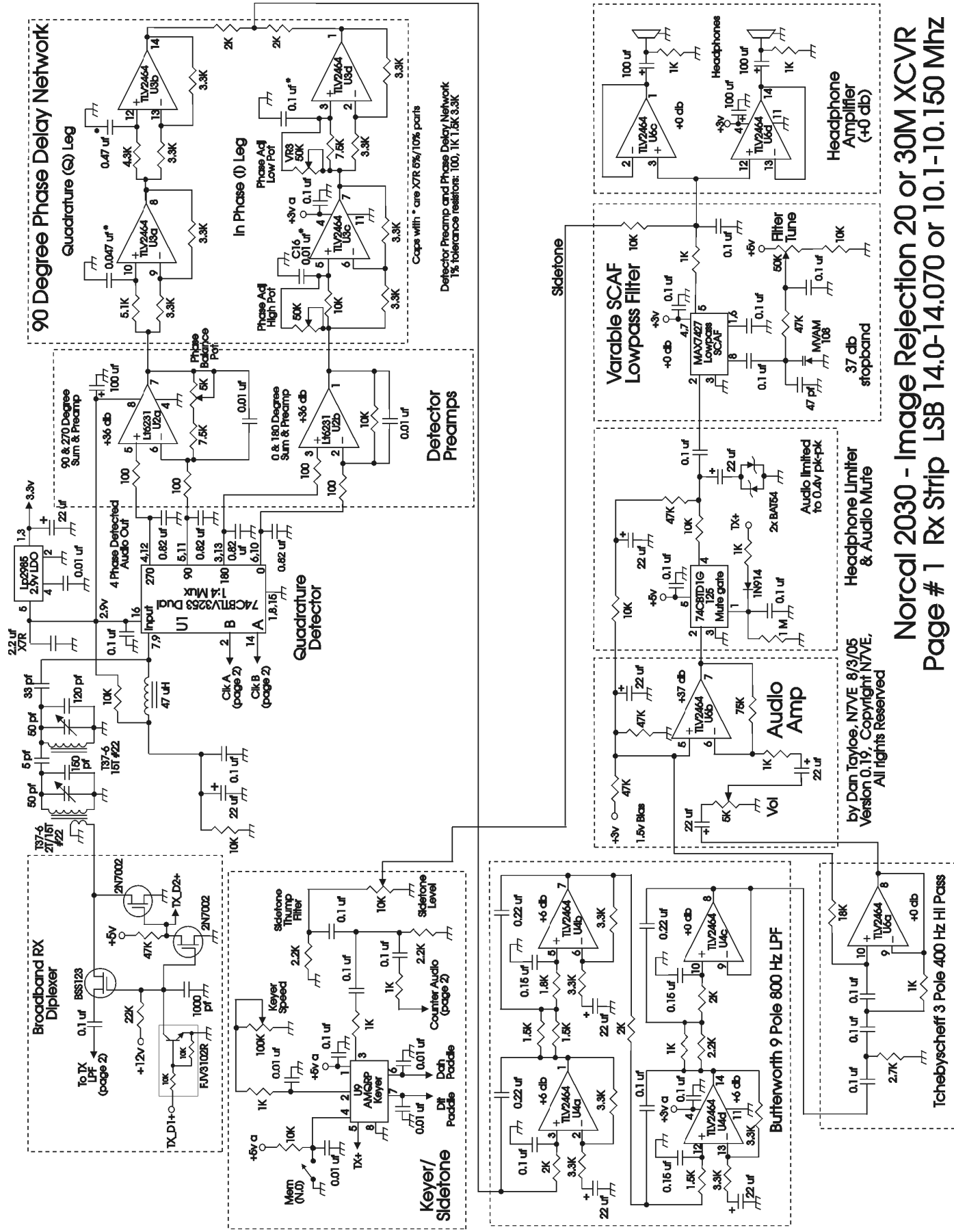

Norcal 2030 - Image Rejection 20 or 30M XCVR
Page # 1 Rx Strip LSB 14.0-14.070 or 10.1-10.150 Mhz

Quadrature Detector

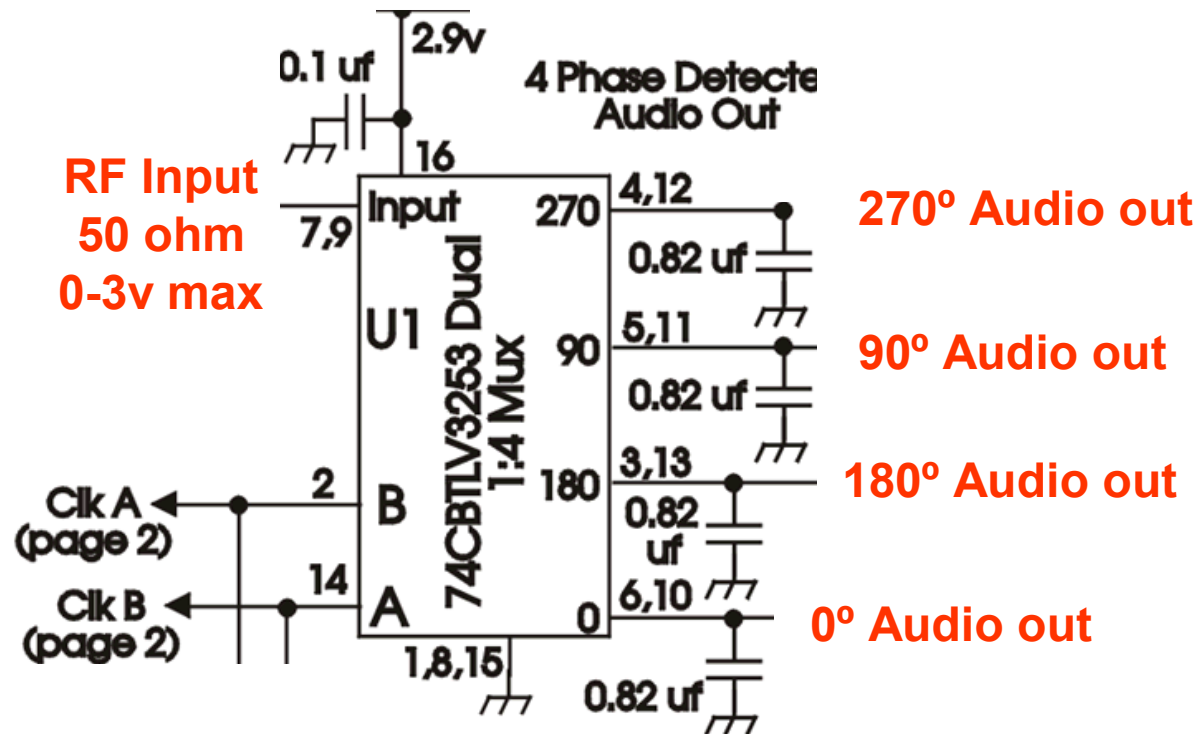


One 50 ohm input,
Four 200 ohm outputs
No power gain

Output ~0.9x Input
due to integration
on detector caps
~0.9 db loss

Diode mixer : *6 db* of
conversion loss typical


- Clocks route RF input to 1 of four Detector Caps at a 4x rate
- Each det. cap. averages $\frac{1}{4}$ cycle of RF – *Audio!*
- Four blade ceiling fan w/ strobe light analogy

Quadrature Detector Outputs

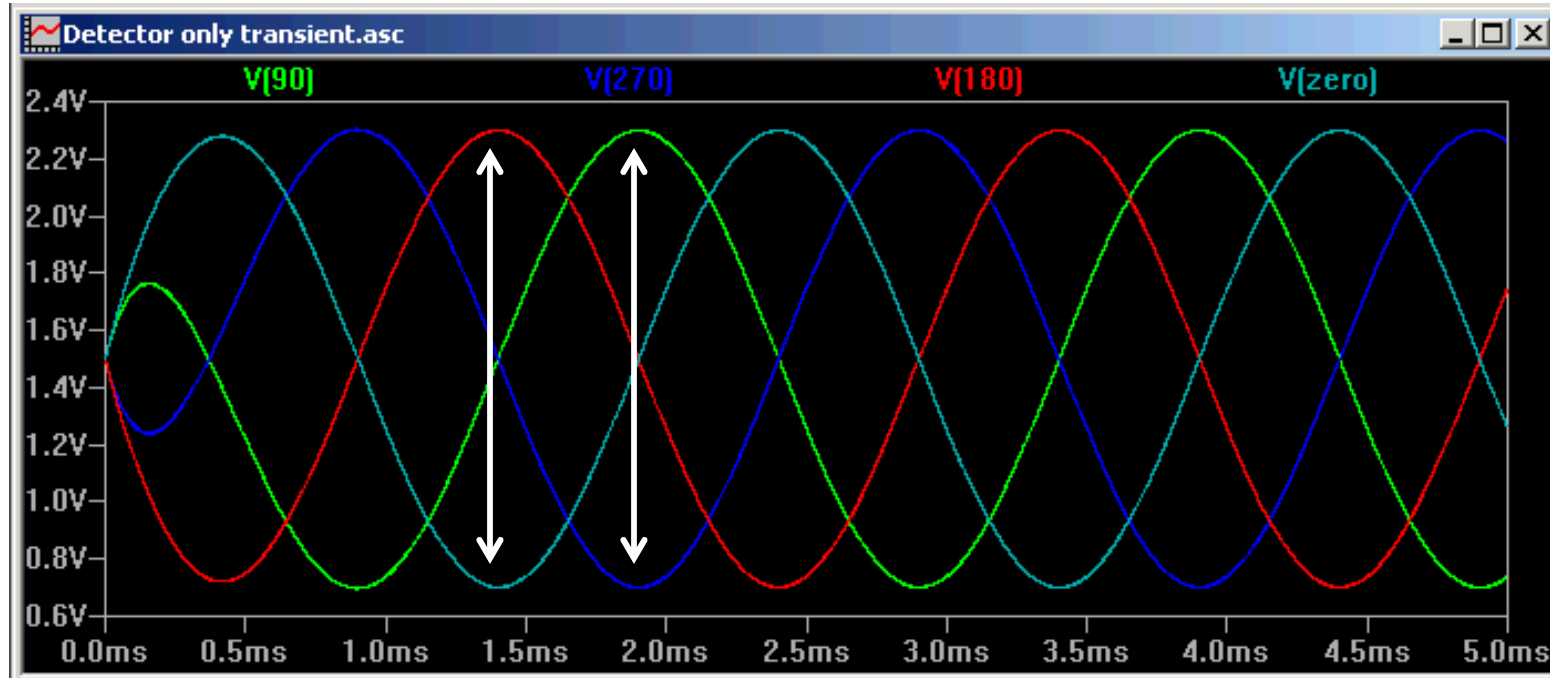

- Note that 0° & 180° and 90° & 270° outputs are *mirror images* of each other.
- These pairs (such as 0° & 180°) are summed *differentially* via + & - inputs of op-amps


NC2030 5 KHz Blocking Calculations

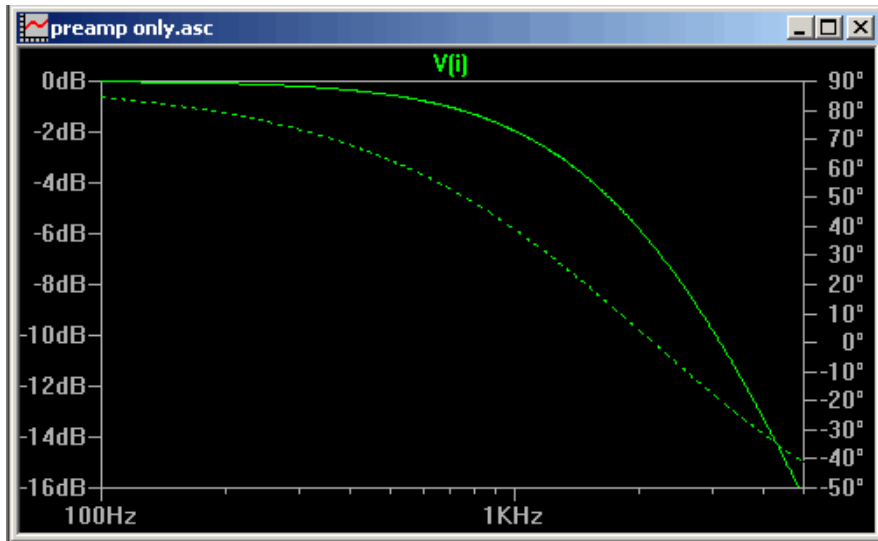

- The simple RC roll off of the Detector and AF preamp is somewhat gradual, but 16 db of attenuation greatly helps BDR (and IP3DR also)


- AF Preamp has 66x of voltage gain (**36 db**)
- **16 db** roll off at 5 KHz leaves 20 db of gain (**10x**)
- With 3v pk-pk max audio output, RF input blocks at **0.3v (-6 dbm)** 5 KHz away
- Using -135 dbm sensitivity, $BDR = 135 - 6 = 129$ db
- **Actual measured result 128.5 db BDR at 5 KHz**

Detector Clock Drive

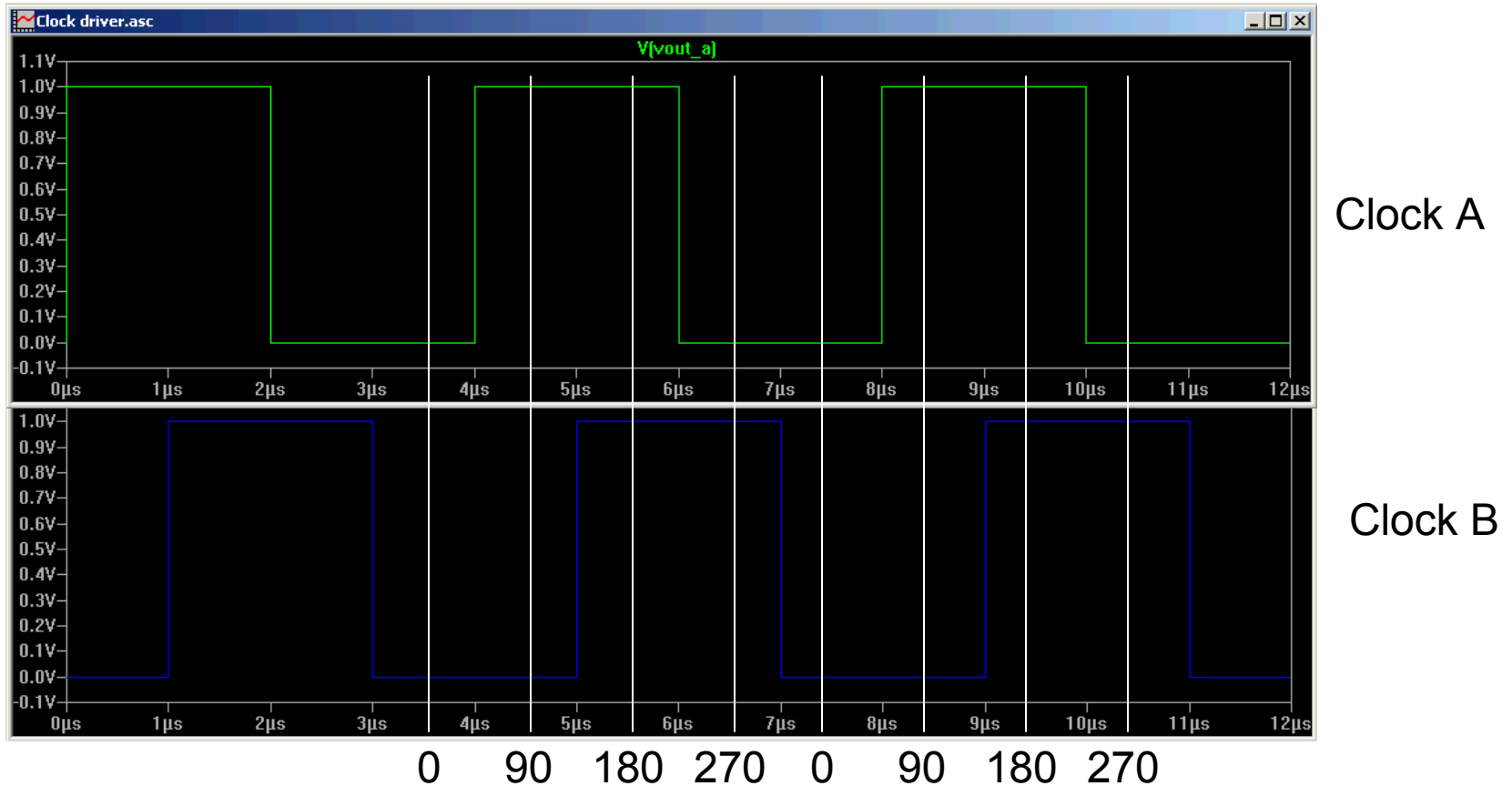


- Need to switch to *each of four* outputs every RF cycle, $\frac{1}{4}$ cycle dwell time on each detector output
- Two phase clock used to get *four output states*

Detector Clock Drive Circuit A

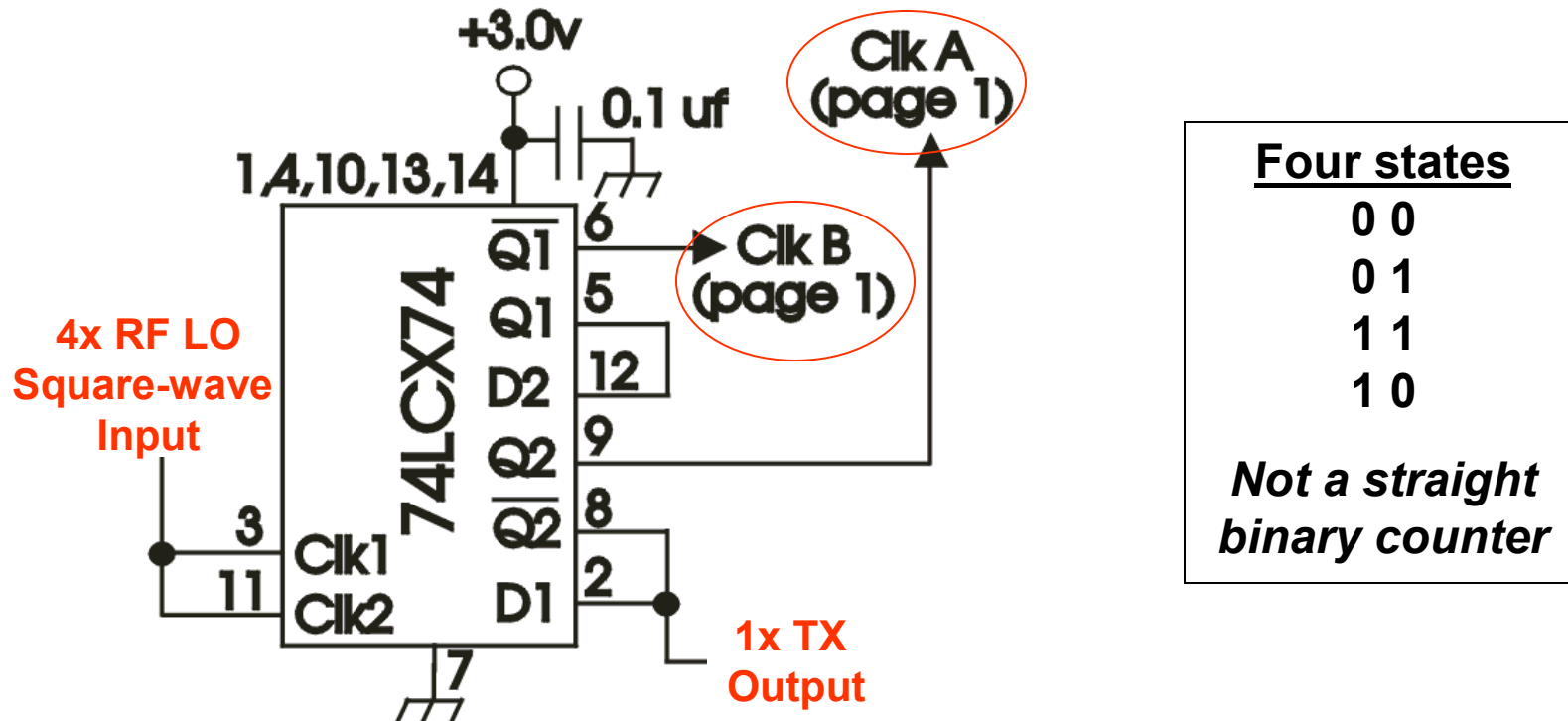


- **4x frequency source** used with digital dividers
- Advantage: Accurate clocks, **excellent opposite sideband rejection over a very wide range**
- Disadvantage: Dividers are a bit **power hungry**

Clock Drive Circuit B (NC2030)

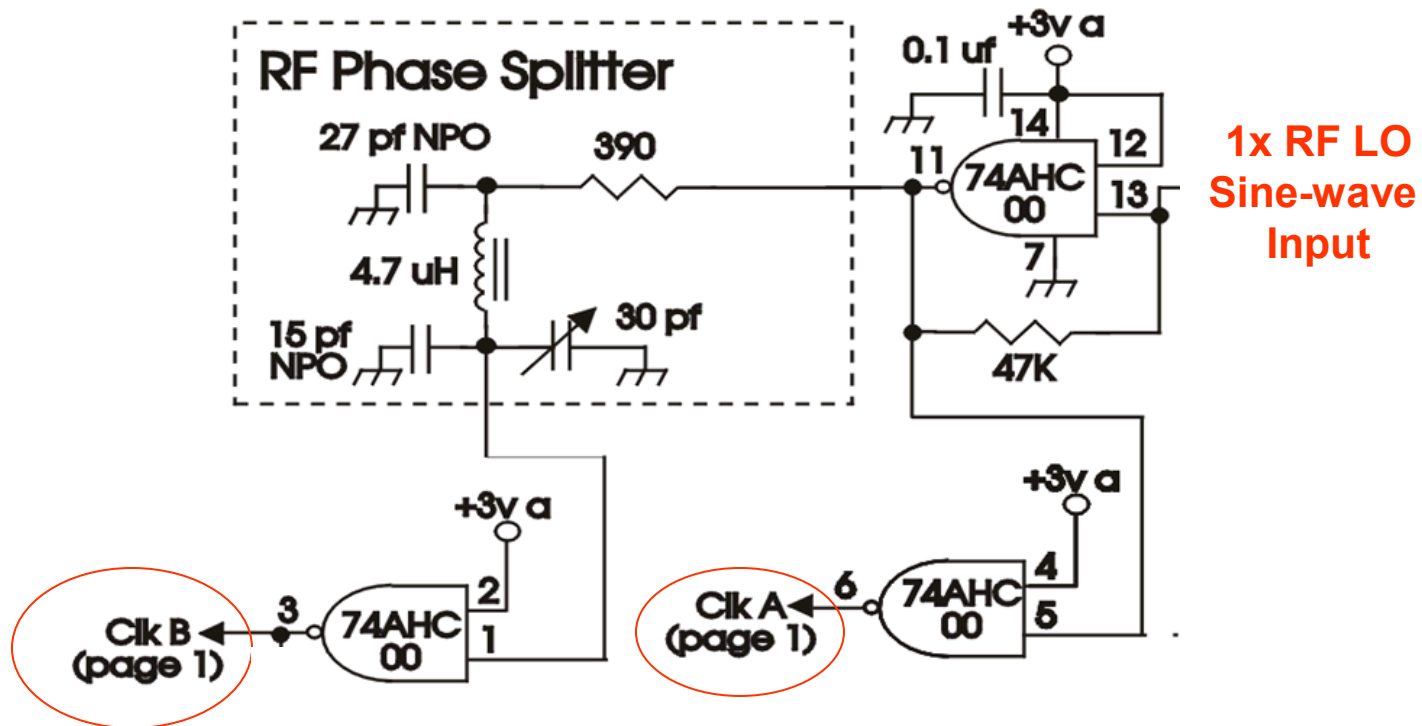


- **1x frequency source** used with L/C delay section
- Advantage: **Uses much less power** than dividers
- Disadvantage: Bandwidth limited, **USB rejection good over a limited range** (i.e., CW portion of band)

I – Q USB and LSB Outputs

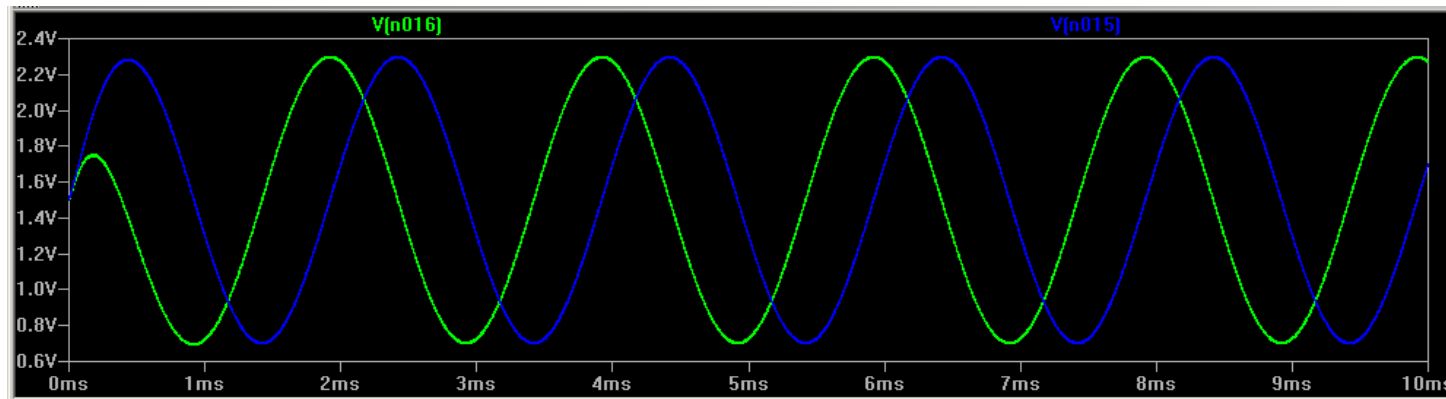


USB
I, Q

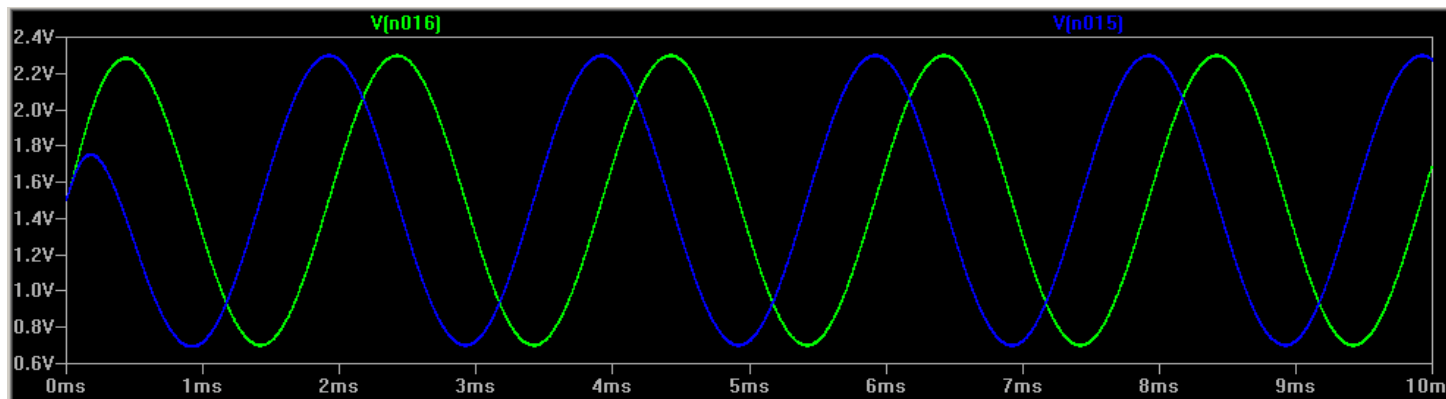

LSB
I, Q


- I (0° , 180°) and Q (90° , 270°) are **90 degrees** apart
- USB/LSB depends on which **leads the other**

90° Shift Phasing Network

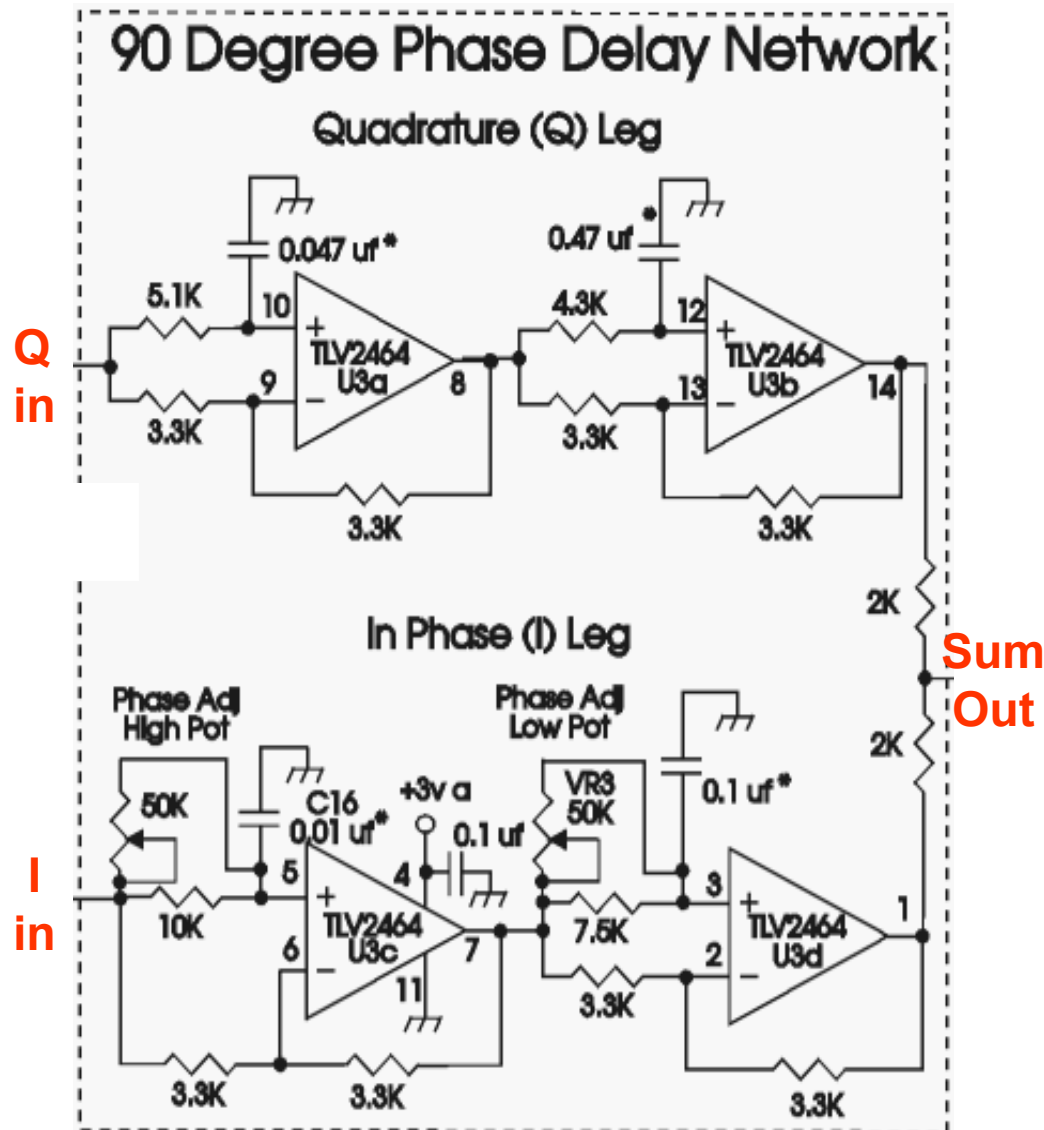


- Two stage R/C phase shift network
- *Both sides cause phase shift*
 - One side starts first
 - 2nd trails 1st by 90°
- Limited sideband rejection range
- *Rejection range optimized for CW bandwidth (500 Hz)*

Phasing – How to Get 90° Shift

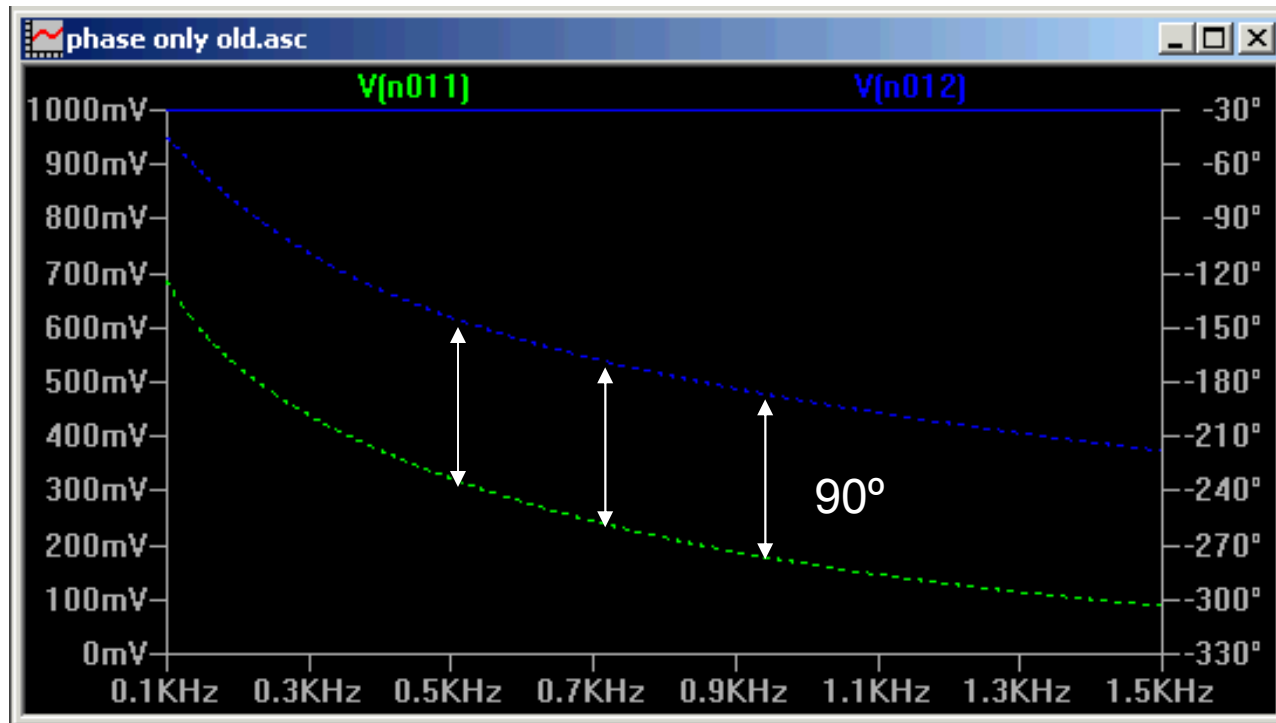

- One side starts falling in phase after the other
- *The late side is adjusted to be exactly 90° late*
- The 90° difference is good for a *limited range*

USB After 90° Phase Shift

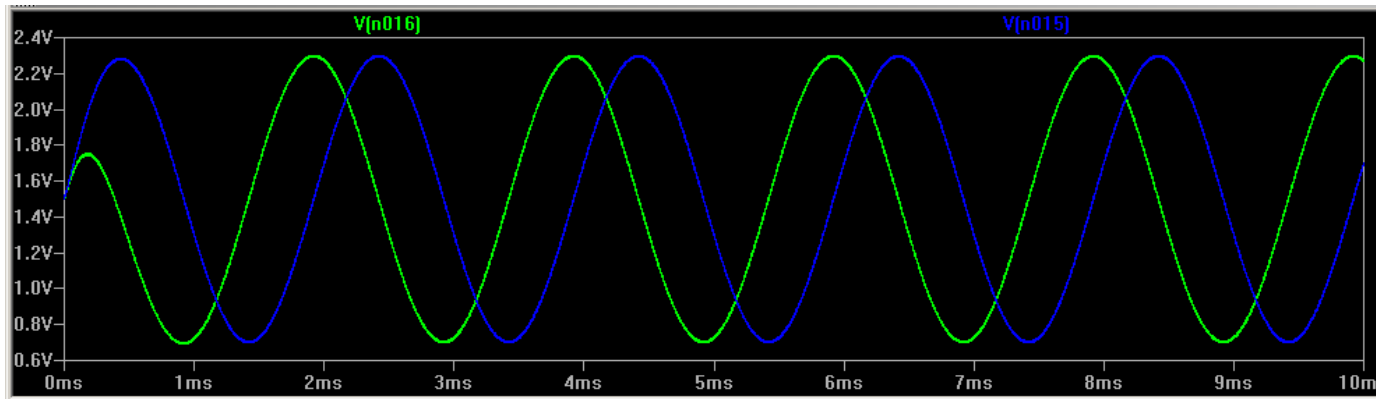


***USB I,Q
before
phasing***




***USB I,Q
after
phasing***

- ***After phase shifting, I & Q opposites of each other***
- ***Phasing outputs sum to zero – USB suppressed***


USB Rejection Plot

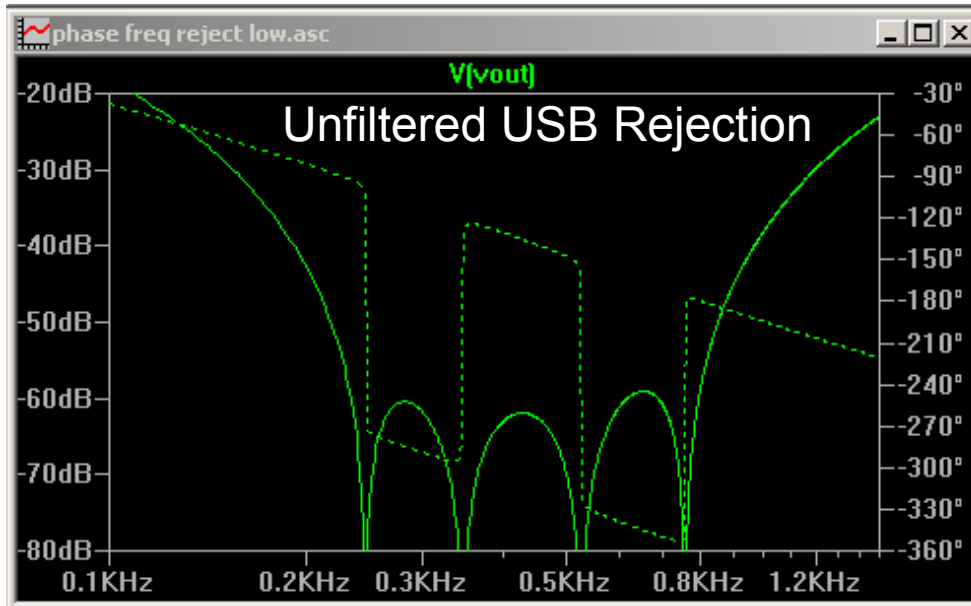

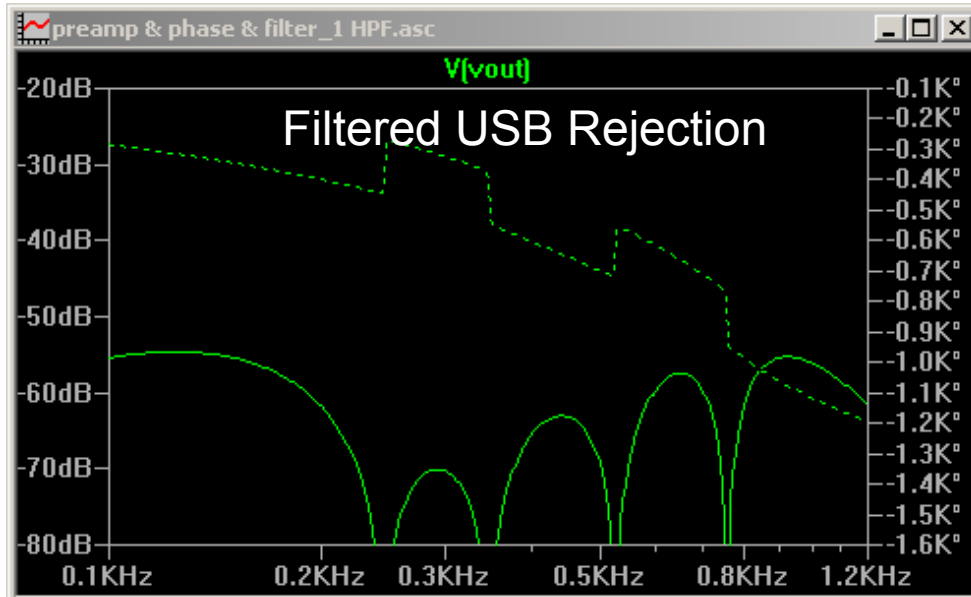
- USB rejection *varies* across audio bandpass
- Smallest USB rejection at 150 & 650 Hz, ~ *55 db* down
- Filtering improves high & low frequency rejection
- Rejection shown is best case
 - LO clock uses L/C phasing
 - *Causes USB rejection to vary across band*
 - > *45 db across the band typical*



LSB After 90° Phase Shift

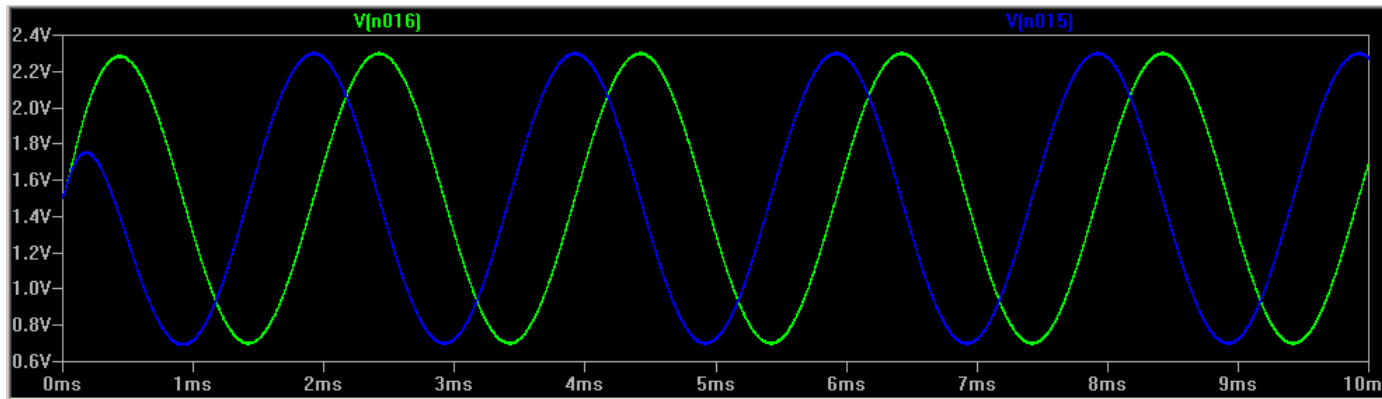

***LSB I,Q
before
phasing***

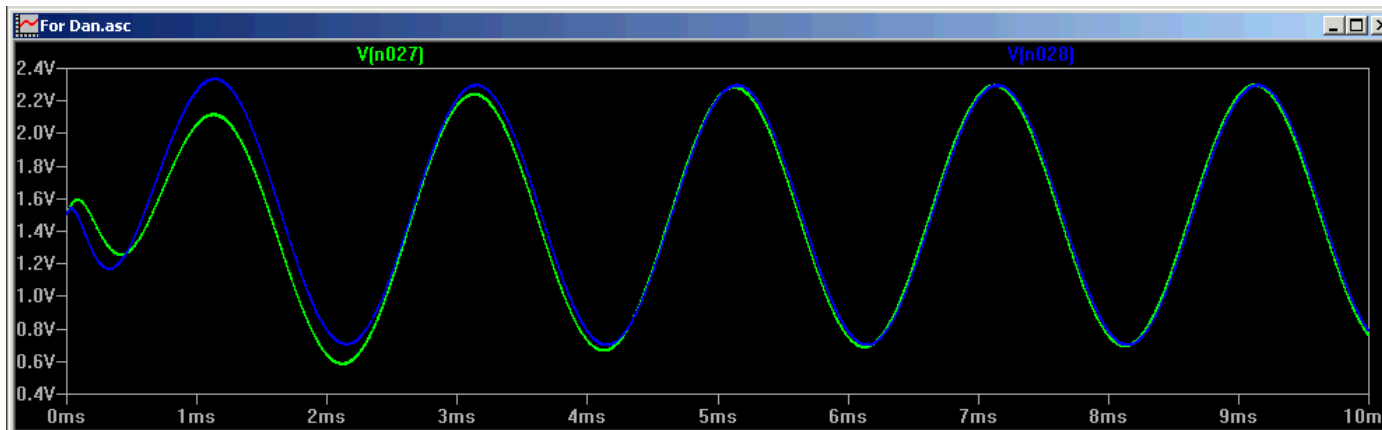


***LSB I,Q
after
phasing***

- ***After phase shifting, I & Q are in phase***
- ***Phasing outputs sum to 2x – **LSB enhanced*****

LSB Audio Response Plot



SCAF LPF not included

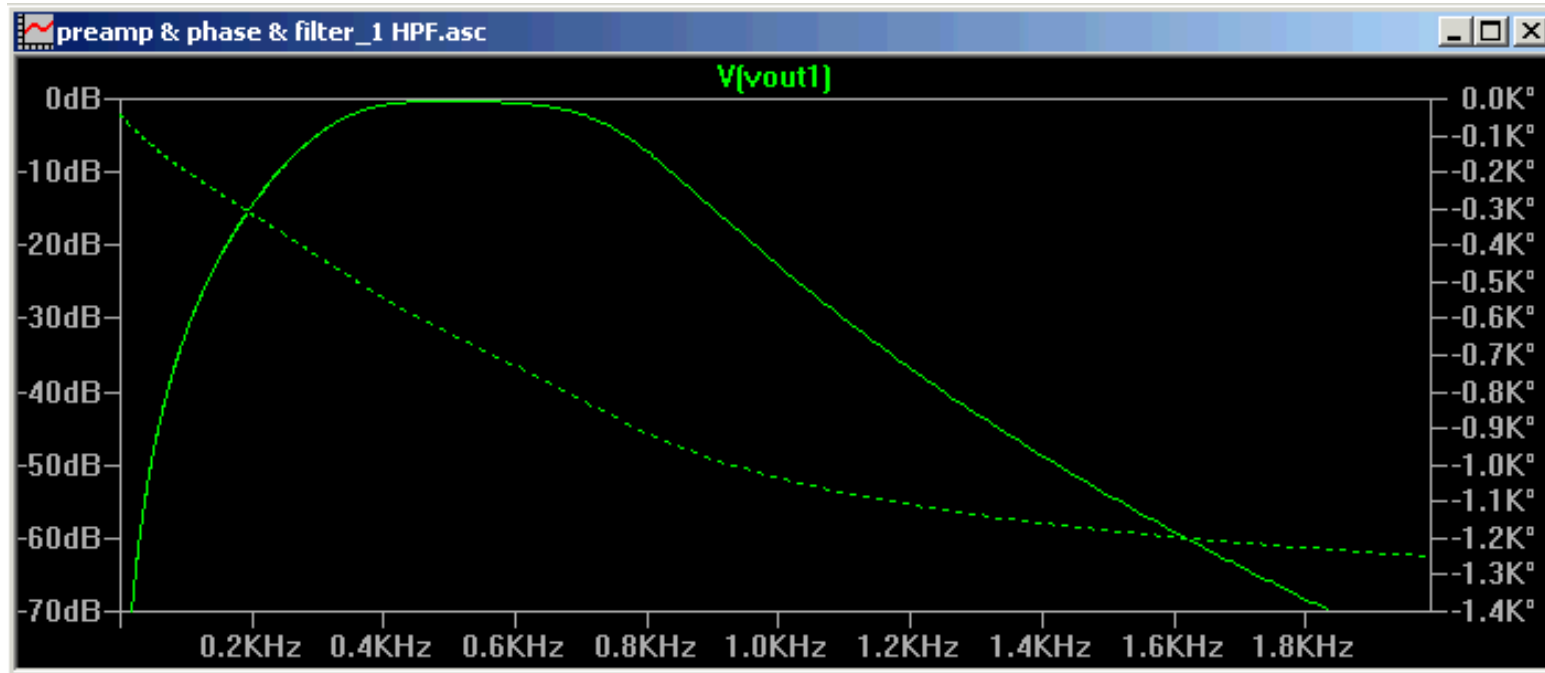

- 6db at 350 & 800 Hz; 60 db at 50 Hz & 1.6 KHz
- Does not include the additional 40 db of variable SCAF LPF attenuation
- *Main RC filter designed for low audio ringing*

LSB Audio Response Plot

Actual Band Noise – 30m

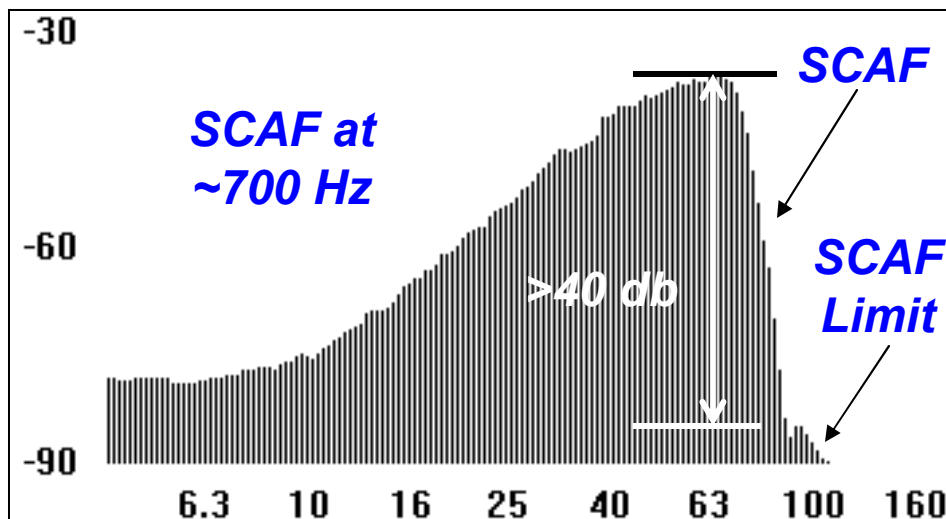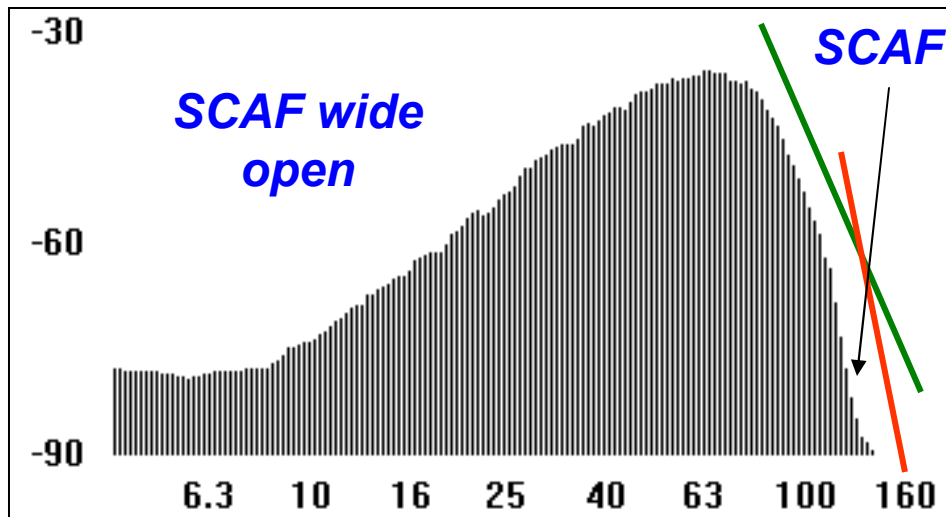

- High side audio roll off is very step
- SCAF cleans up high frequency roll off even when “wide open”
- SCAF very good at removing a high side interferer when needed
- *Noise below 100 Hz is a sound card issue*

DC Receiver Pwr Consumption

- Quadrature detector **voltage** driven not **power** driven as required by diode mixers.
 - 74CBTLV3253 is a dual 4:1 analog bus switch
- First low noise audio preamplifier outputs are **voltage** outputs, not **power**, as needed by superhets
- **3v** receiver powered by a 3v & 5v switching supply, giving a **3x power savings** over simple linear regulation from 12v

DC Receiver Pwr Consumption

- VFO and VXO; 3 ma
- LO mixer; 1.6 ma
- LO filter amp; 9.5 ma
- LO squaring & detector driver (74AHC00); 0.8 ma
- Quadrature detector (“Tayloe Mixer”); 4.4 ma
- First audio LNA & phase shift network; 7.8 ma
- High and low pass RC filters and headphone drivers; 2 ma
- SCAF variable audio low pass filter; 1 ma

=> Roughly **30 ma** total receiver drain at **3v** supply
- **14 ma** for the **LO subsystem**, **16 ma** for the **receiver line up**

=> **11 ma at 12v** into the 3v & 5v switching supply

Conclusions

DC receivers have a performance advantage over superhets because:

- 1. *DC quadrature det has lower loss (1 vs. 6 db)***
 - DC does not need an RF amp for high sensitivity
- 2. *DC detector has a limited ~1.5 KHz bandwidth***
 - The superhet mixer can be 100's of MHz wide
- 3. *DC AF amp also has ~1.5 KHz bandwidth***
 - The superhet has a wide bandwidth IF amp (>1 MHz?)
- 4. *DC receiver uses R/C active filters, not crystals***
 - Superhet good to ~2v pk-pk because of its crystal filter
 - DC filter is good to 36v pk-pk signal
 - DC can have superior large signal capabilities (20+ db higher than current 3v NC2030)